

## S5. ACTIVE MATRIX LCD ADDRESSING AND ELECTRONICS

Why AM      Aim of AM      Principles  
Electronic subsystems  
Timing      Waveforms      Kickback

## Why active matrix addressing?

### REVIEW CONSTRAINTS OF PM ADDRESSING

#### Passive matrix is

- (In principle) simple
- Uses low-tech, low-cost backplane technology


#### But due to low duty cycle and crosstalk

- Requires very sophisticated drive waveforms
- Still cannot drive very large numbers of rows
  - Each row of pixels is “intentionally” addressed for at most  $1/n$  of the frame time (where  $n$  = number of rows)
  - Each row of pixels is subject to the data signals that drive the other rows of pixels (for  $(n-1)/n$  of the frame time)
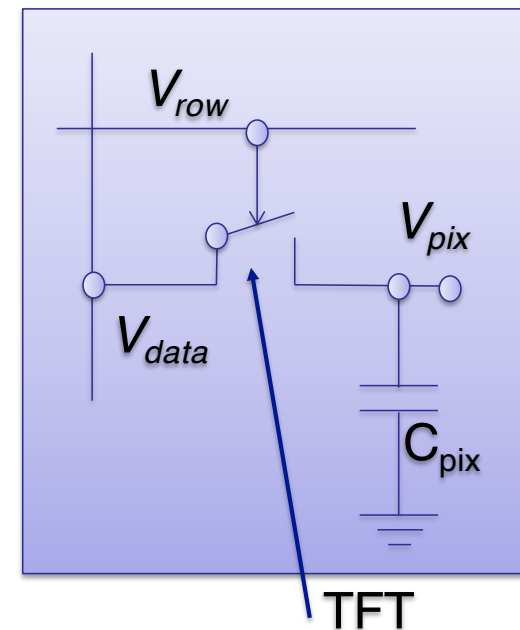
# The Aim of Active Matrix Addressing

The aim of AM Addressing is to overcome the limitations of PM Addressing by

- Increasing the duty cycle
  - Putting the drive signal into the pixel electrode during a line-addressing time and keeping it there for all or most of the frame time
- Reducing cross-talk
  - Isolating the pixel electrode from the effect of signals driving pixels in other rows
- In short we need a non-linear element in each pixel
  - In practice this is frequently implemented as a “sample-and-hold” circuit as show





# Active Matrix

Row and column electrodes on active (back) substrate  
Common electrode on front substrate

Switch = TFT

- Active switch and storage element per pixel isolates electronic addressing of pixel from drive EO element
- Per row / column
  - One driver
  - One connecting wire


Storage Cap = pixel electrode

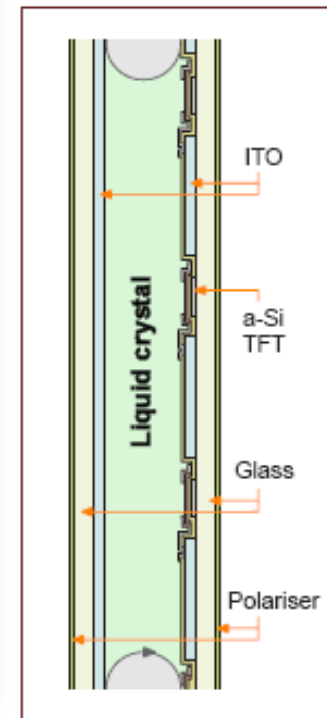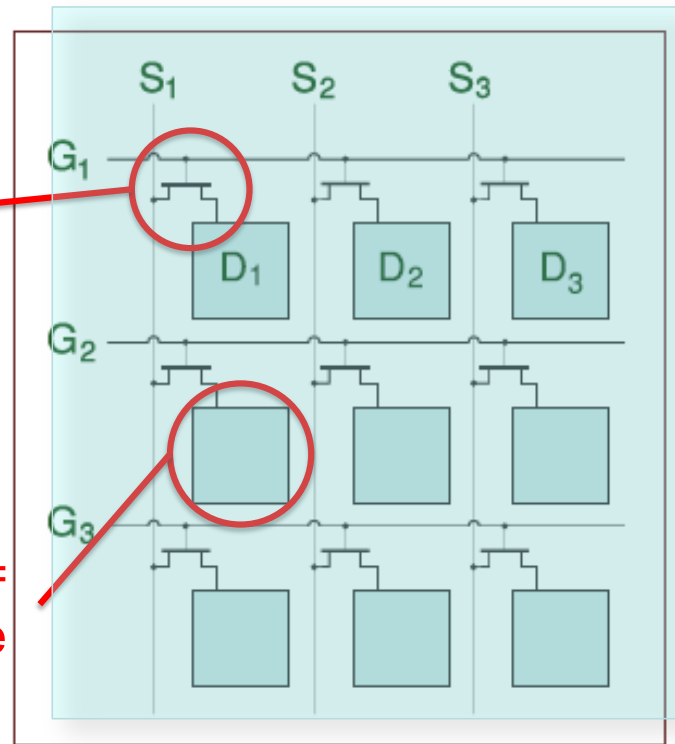

Active matrix LC display


- MxN pixels requires only M+N drivers

## TFT-LCD Exploded View

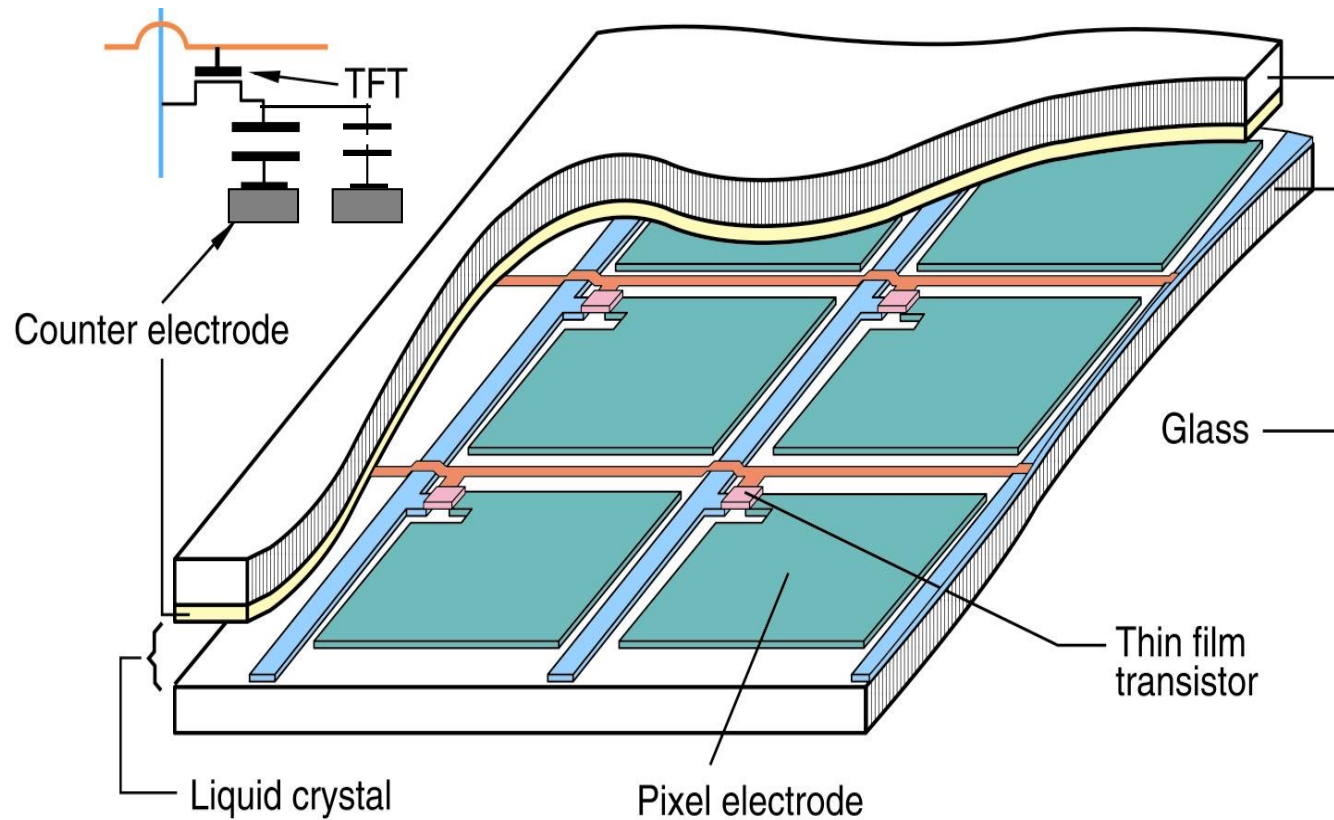

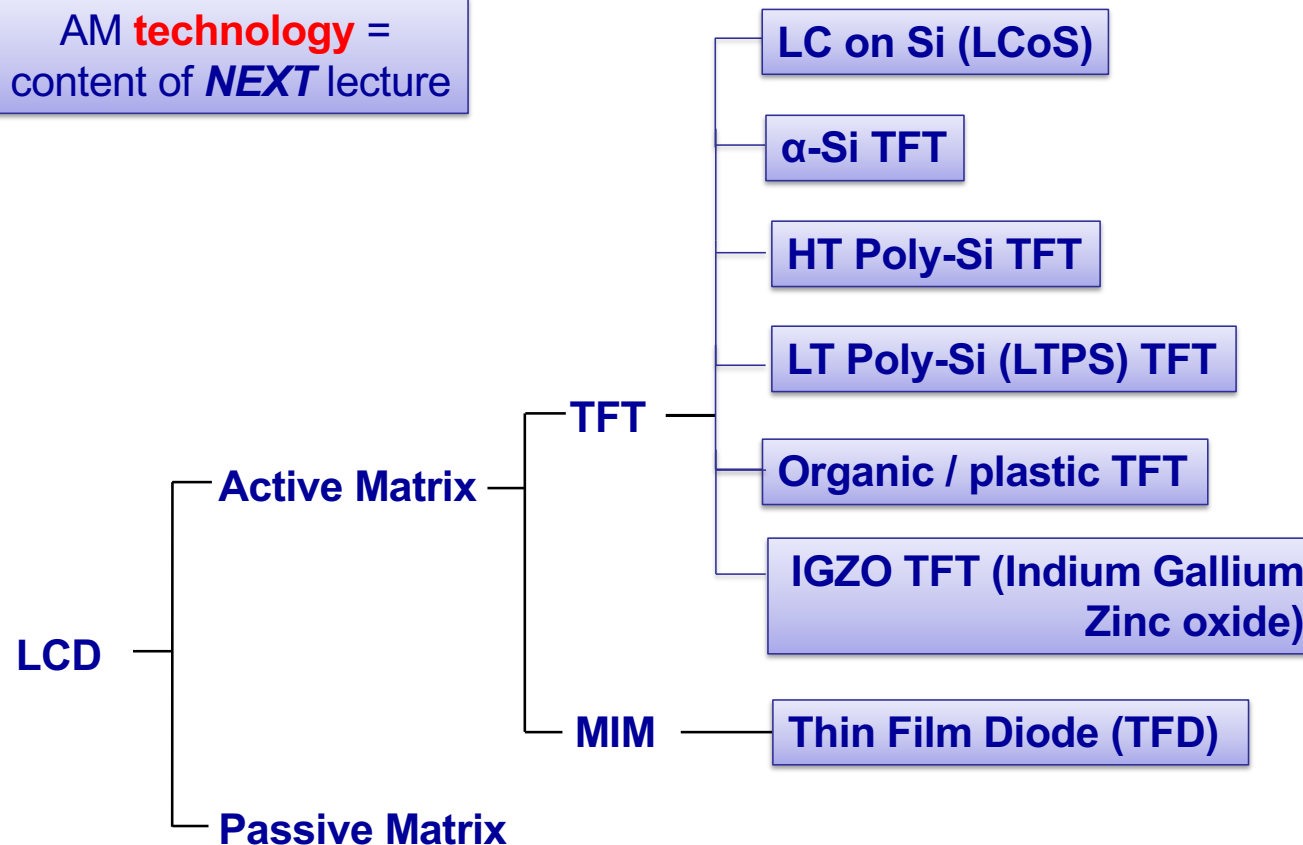
# Active Matrix Technologies

AM **technology** =  
content of ***NEXT*** lecture



# AM Pixel Circuit

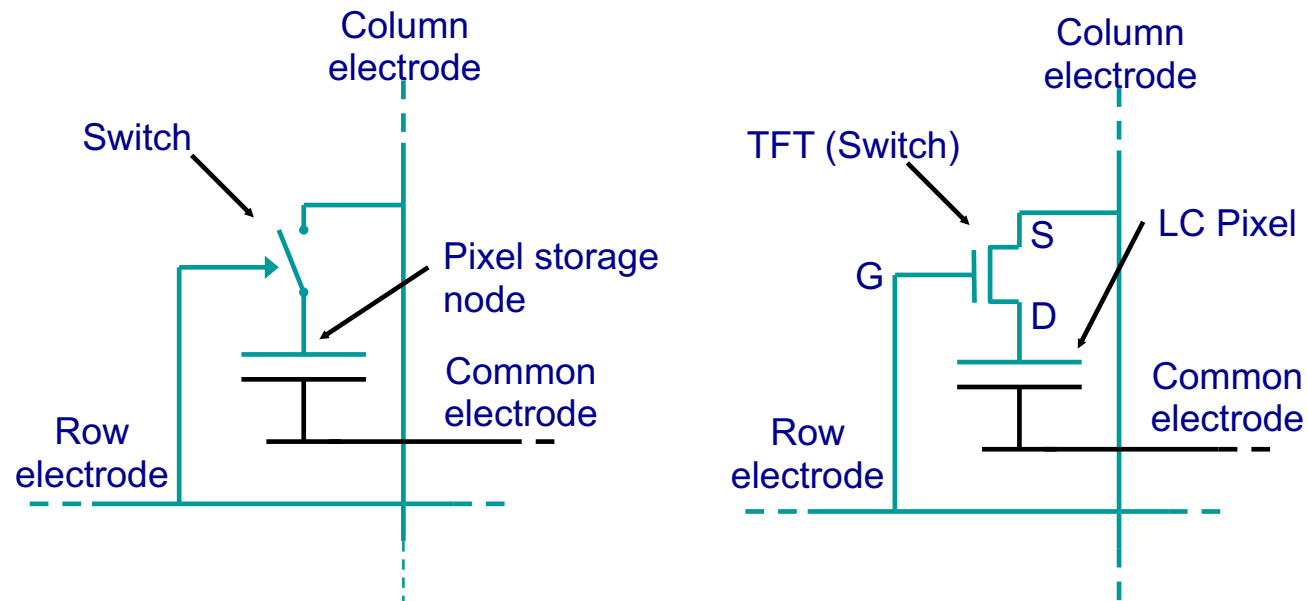


## Active Matrix Addressing

- Reduces crosstalk
- Simplifies addressing waveforms
- Increases pixel drive time from  $1/N$  of field time to  $\sim$  field time
- Allows more rows of pixels

DM-MJR

# Active Matrix Structure

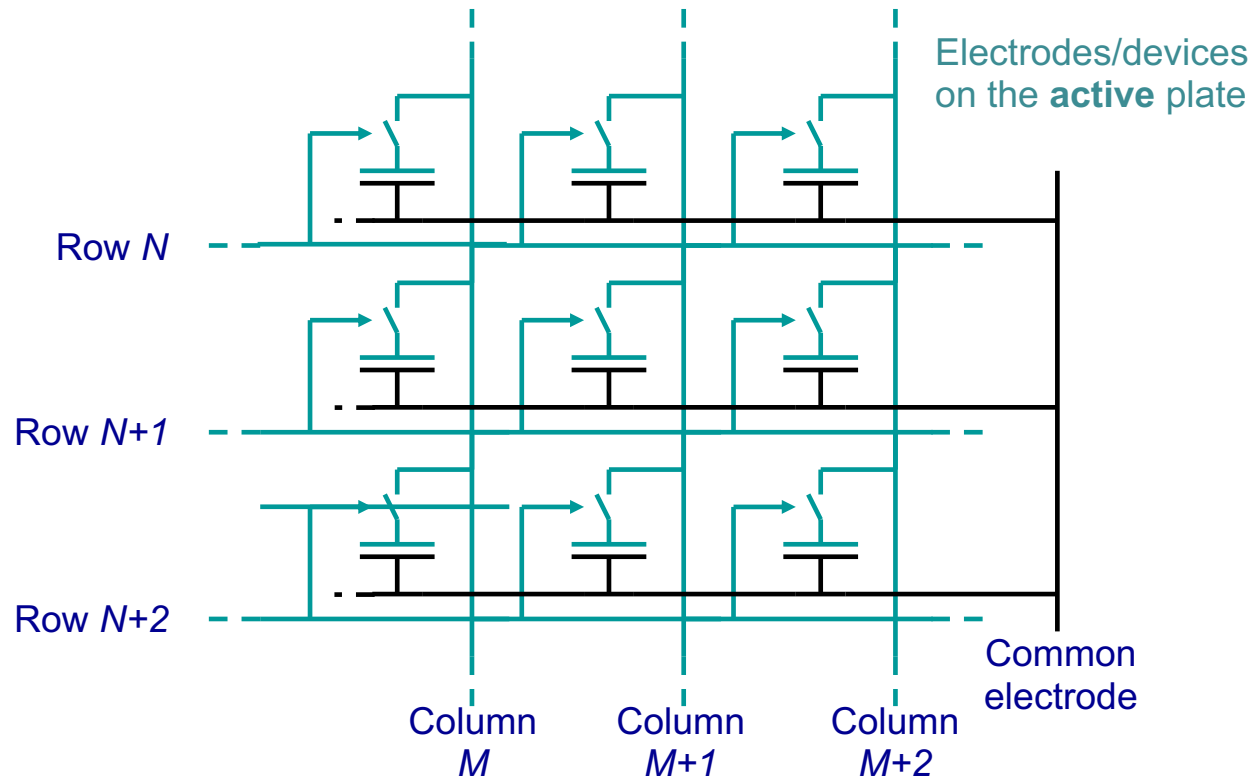



## Row Sequential Addressing 1/5

Each row of pixels is addressed in sequence

Pixel data is applied to the column electrodes


Column data is transferred into a row of pixels

- Achieved by applying a pulse to the row electrode
- Closes the switches (turns the TFTs on)
- Charges up the pixel capacitance,  $C_{LC}$


When pixel is charged the TFT switch is opened

- Pixel capacitance is isolated
- Charge remains on pixel


## Row Sequential Addressing 2/5

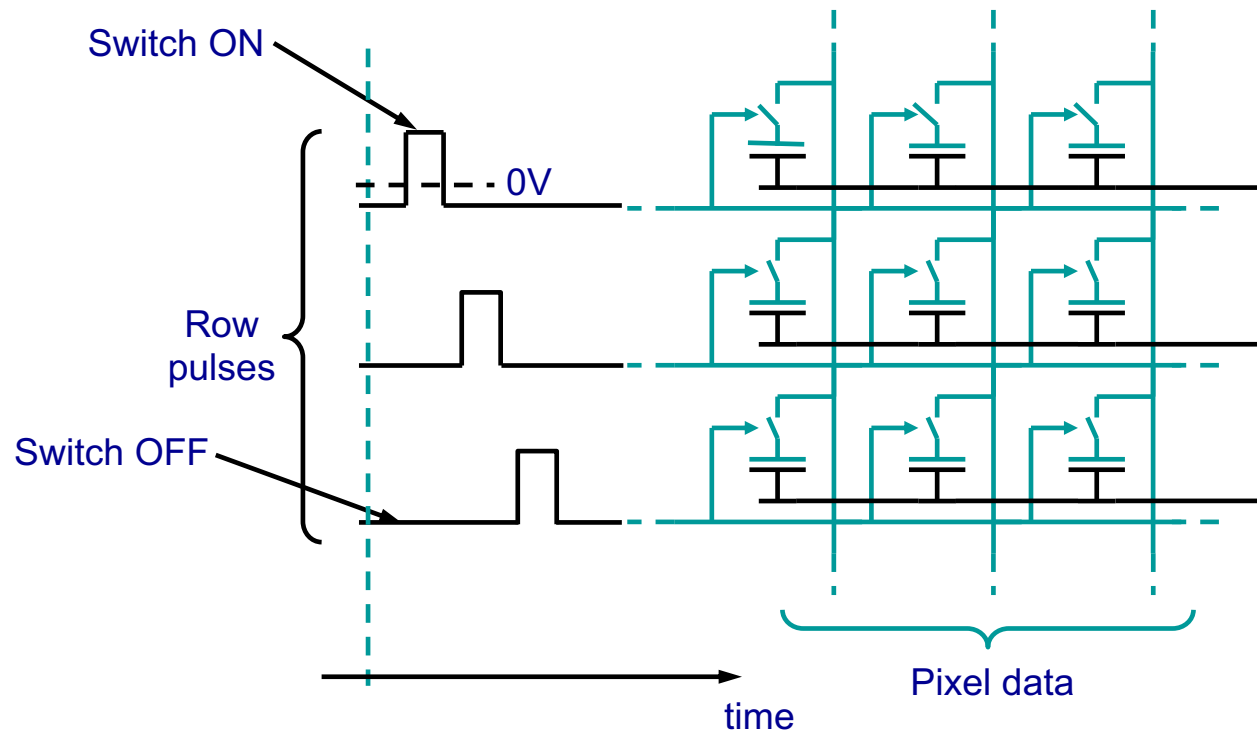


## Row Sequential Addressing 3/5

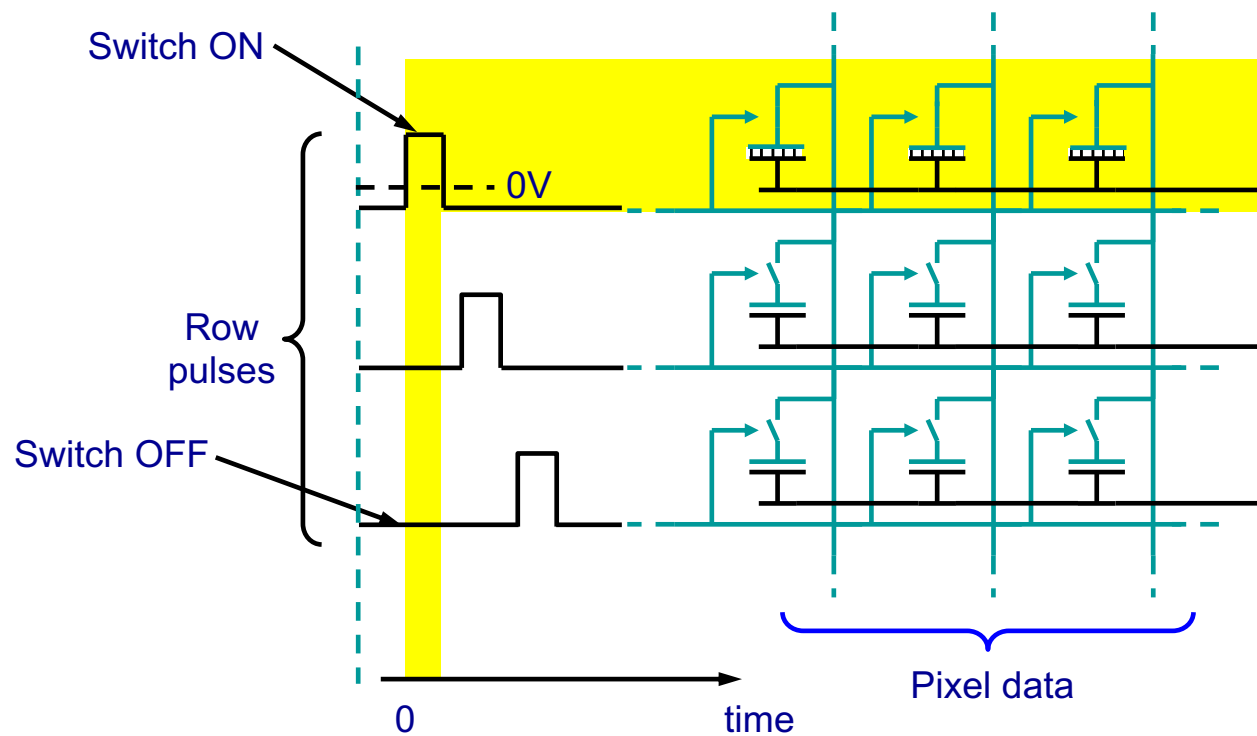



## Row Sequential Addressing 4/5

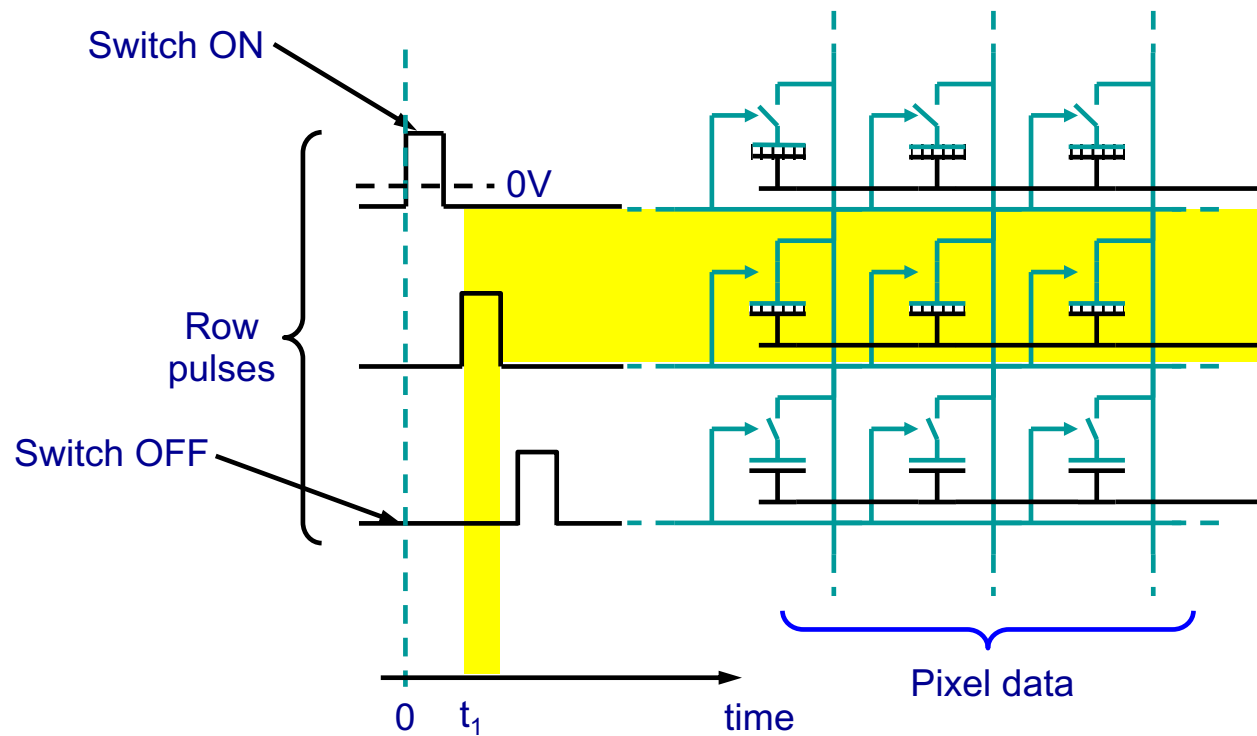

## Row Sequential Addressing 5/5

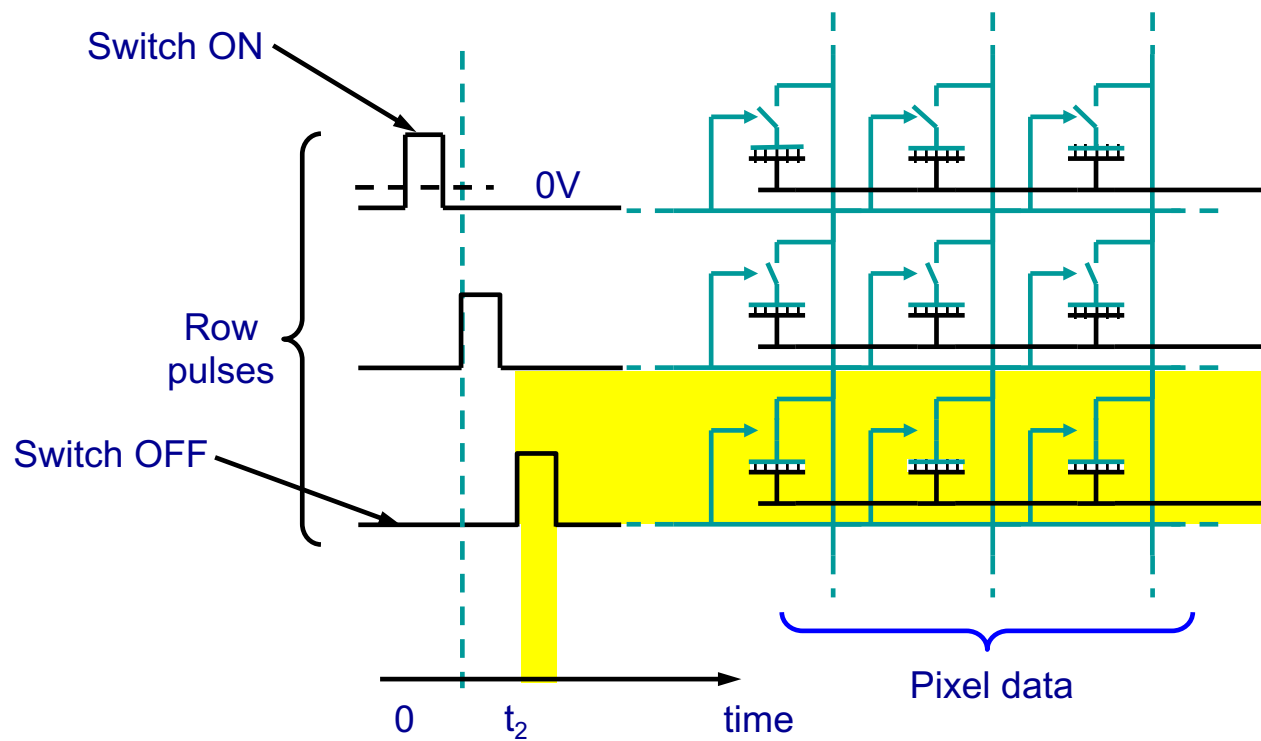


## AM LCD Module (including backlight)

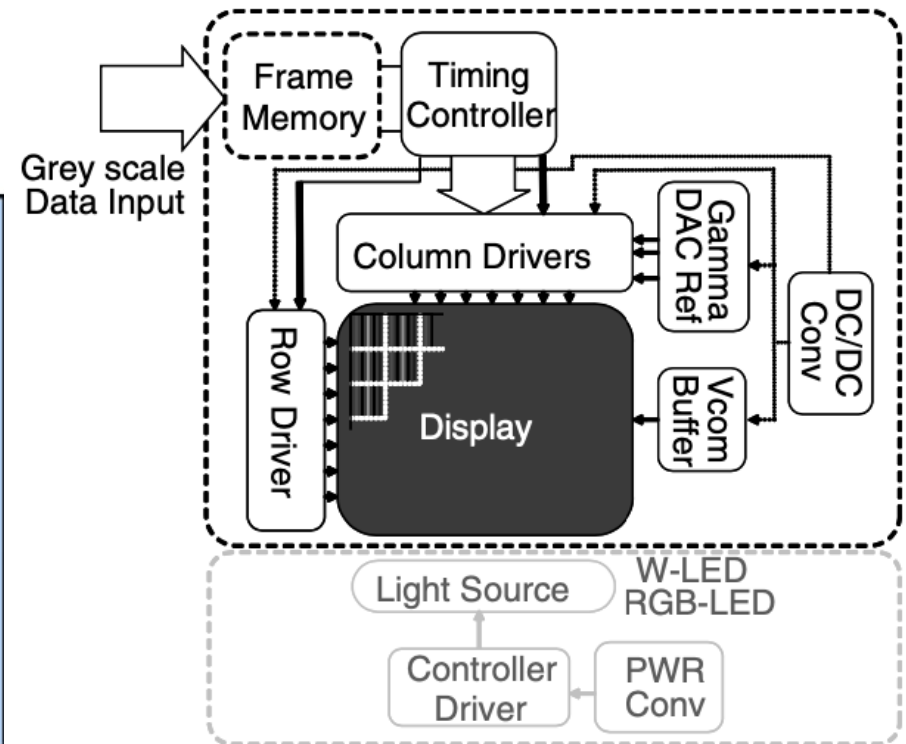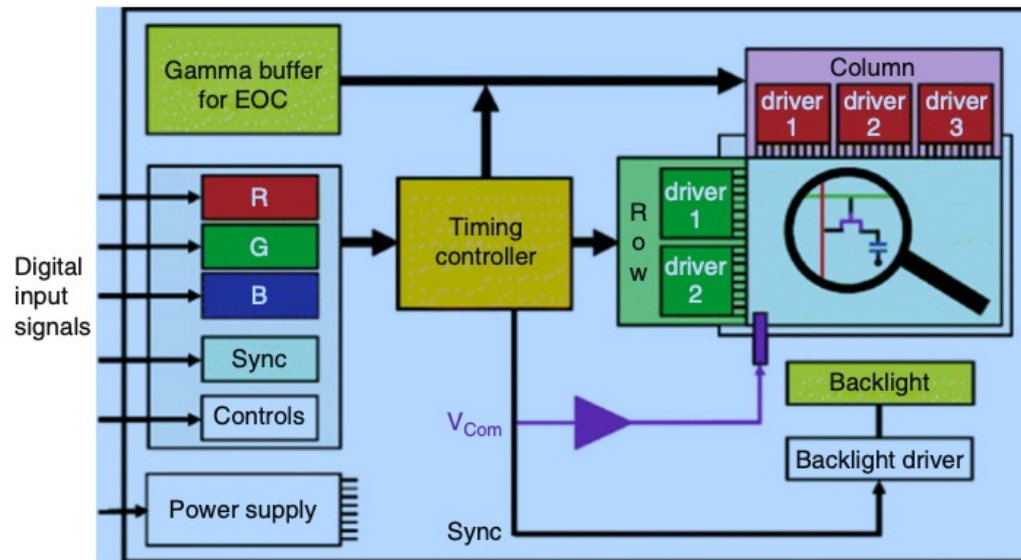


**Figure 9.3** The major functions within an Active Matrix LCD

# Panel Interface Timing

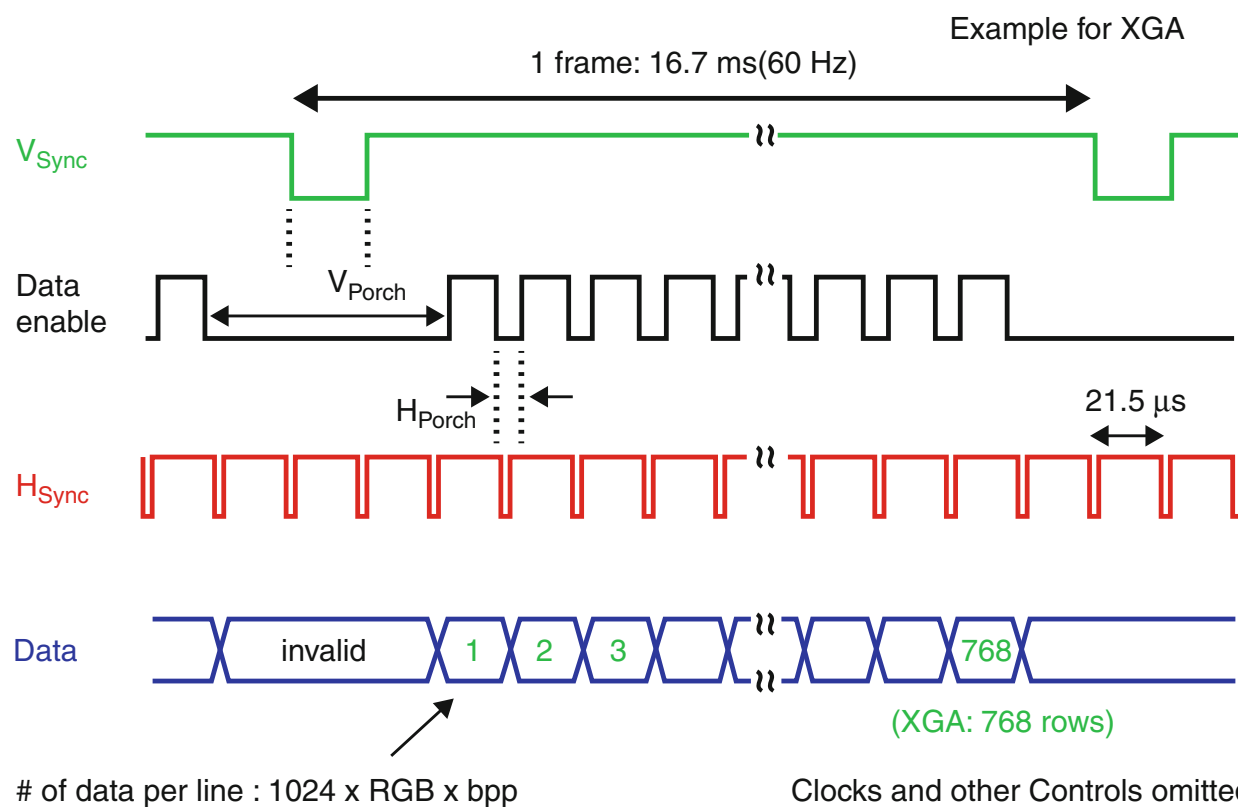

**Fig. 2** Typical example of parallel panel interface timing which is practically the same for Timing Controller data input (for details see section “[Timing Controller and Intrapanel Interface](#)”)


# LCD Timing Controller

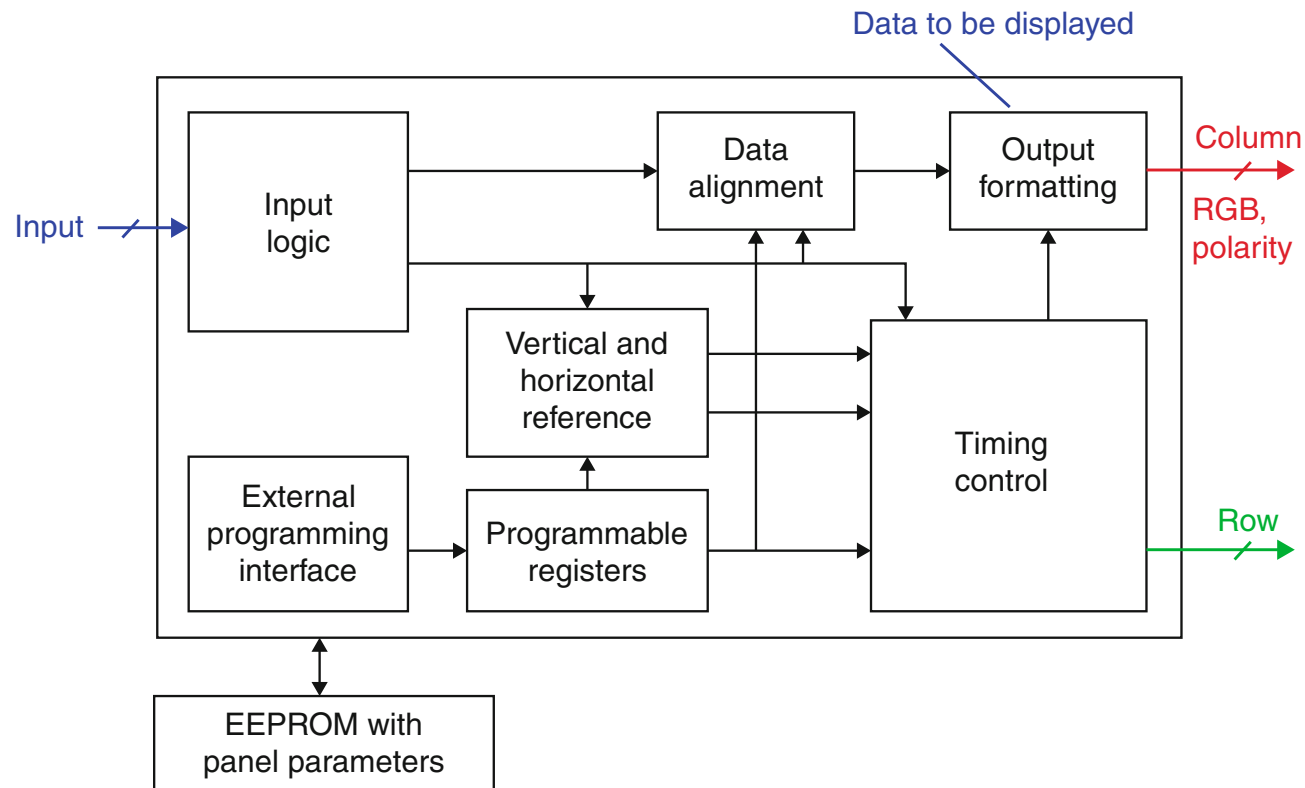

**Fig. 4** Simplified block diagram of an LCD Timing Controller with its inputs and outputs




# Panel Electronics

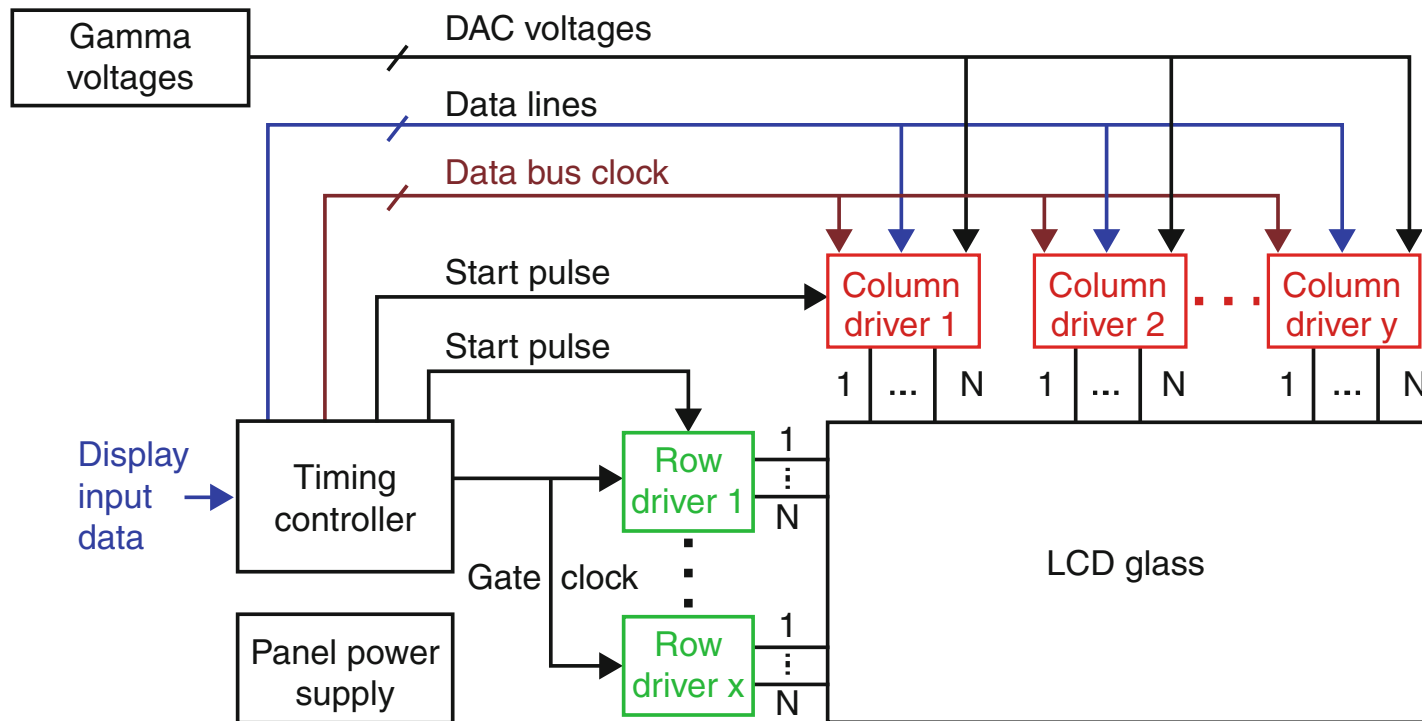

# Data Rates

Resolution /  $10^6$  Pixel

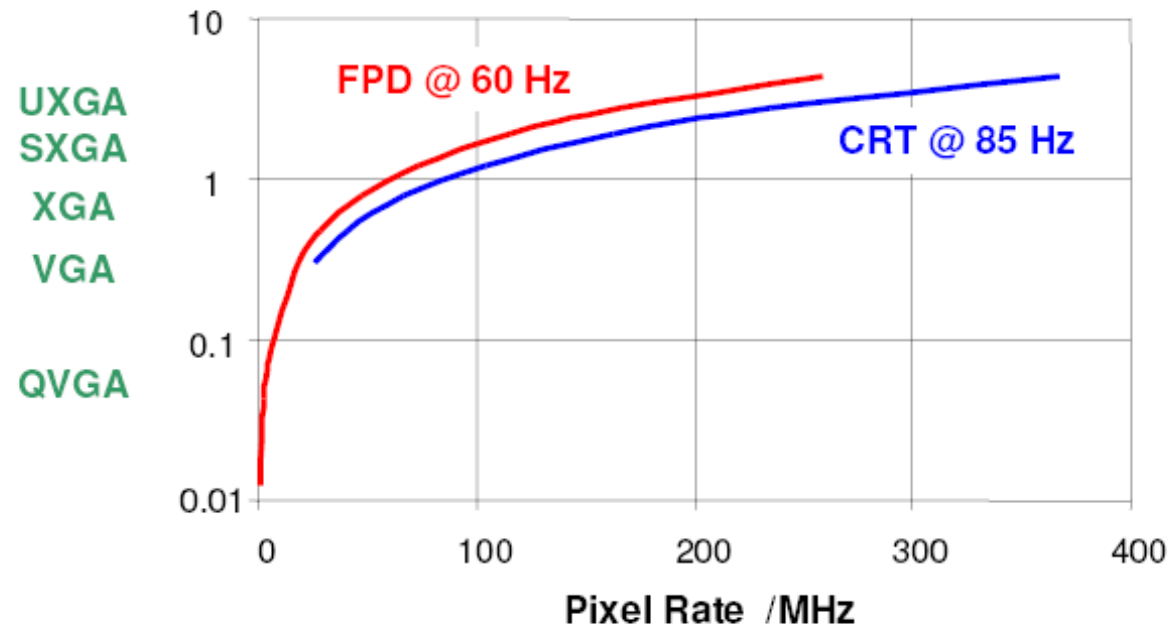

**Pixel frequency** = Resolution x Frame frequency (limit for parallel interfacing)

**Data rate** = Pixel frequency x RGB x Colour depth (limit for serial interfacing)


# Row Driver and Timing

Shift register passes token


Token determines which row is active

Dir sets scan direction

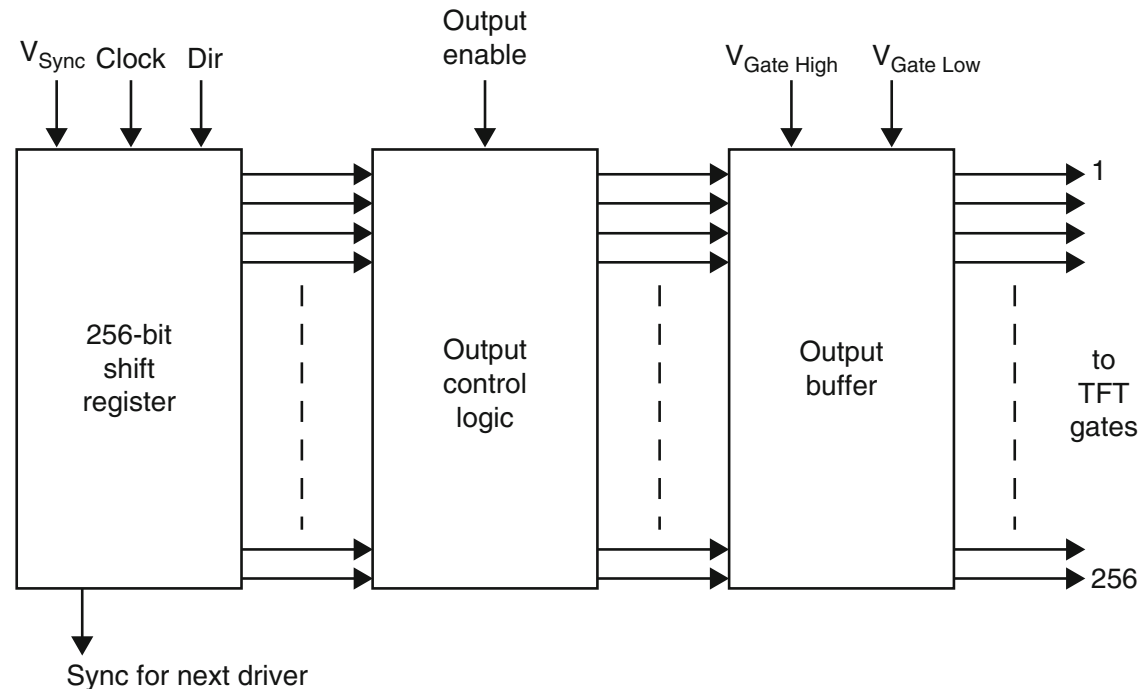
Output enable cuts gate voltage before next line to prevent cross-talk



# Row Driver Timing Diagram

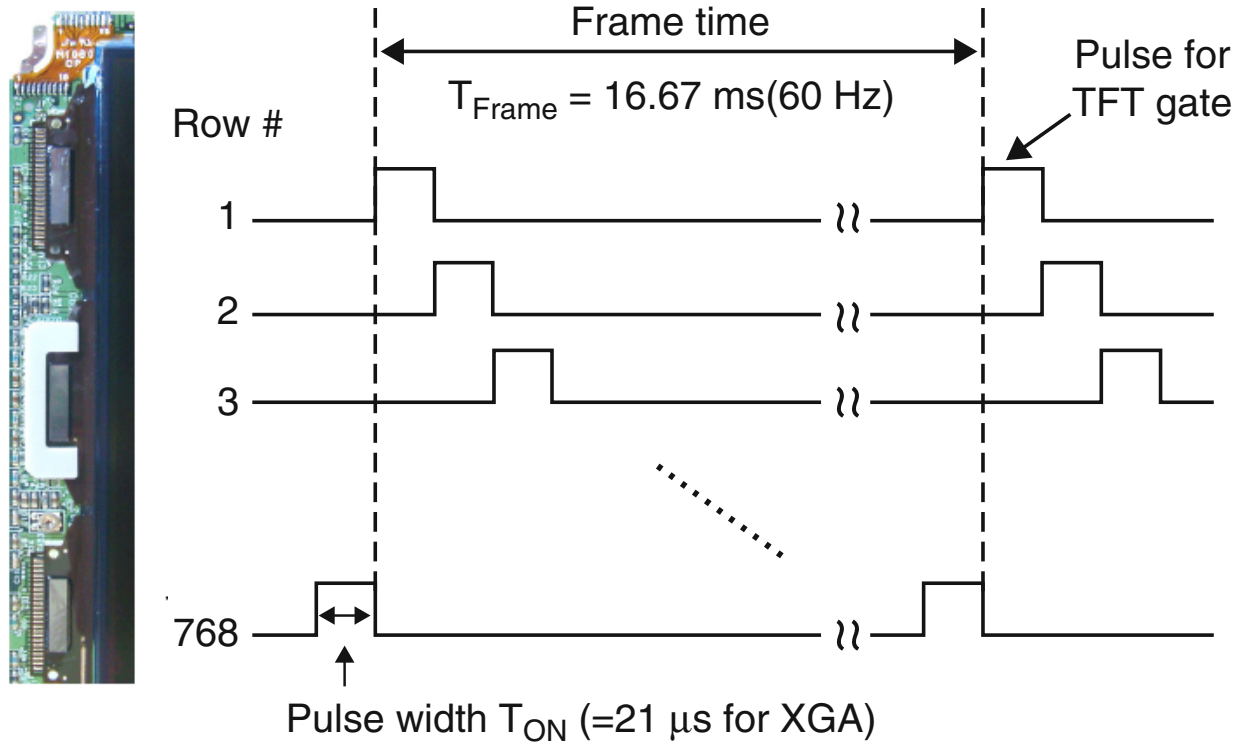

# Row Driver Timing Diagram

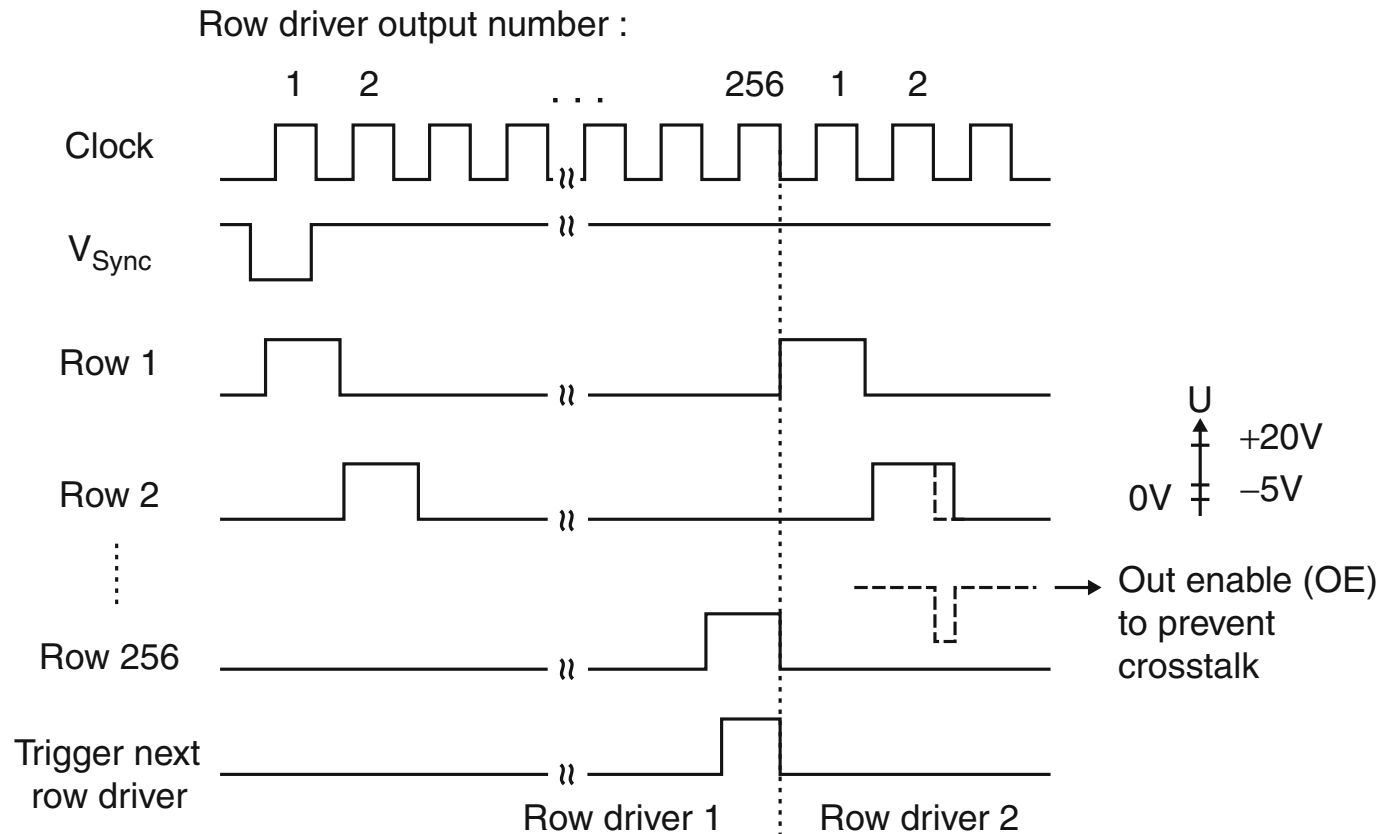

## Example Column Driver

Example shown is

- Digital in, analog out


Could also be

- Digital in, digital out
- Analog in, analog out


Polarity for inversion

$V_{\text{gamma}}$  for EO TF

Clocks etc not shown

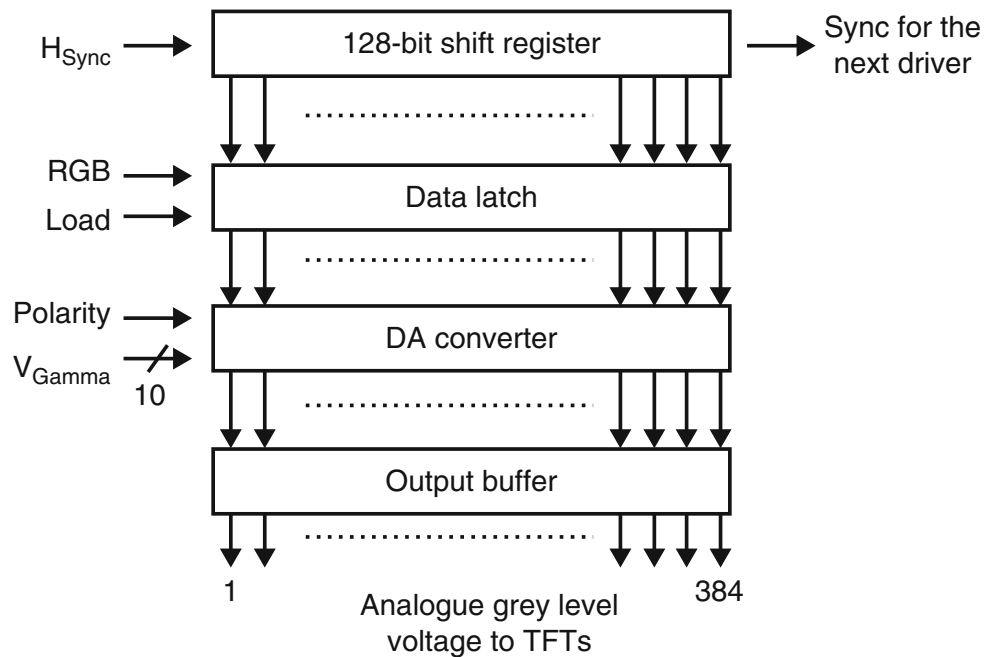


## Column driver timing diagram

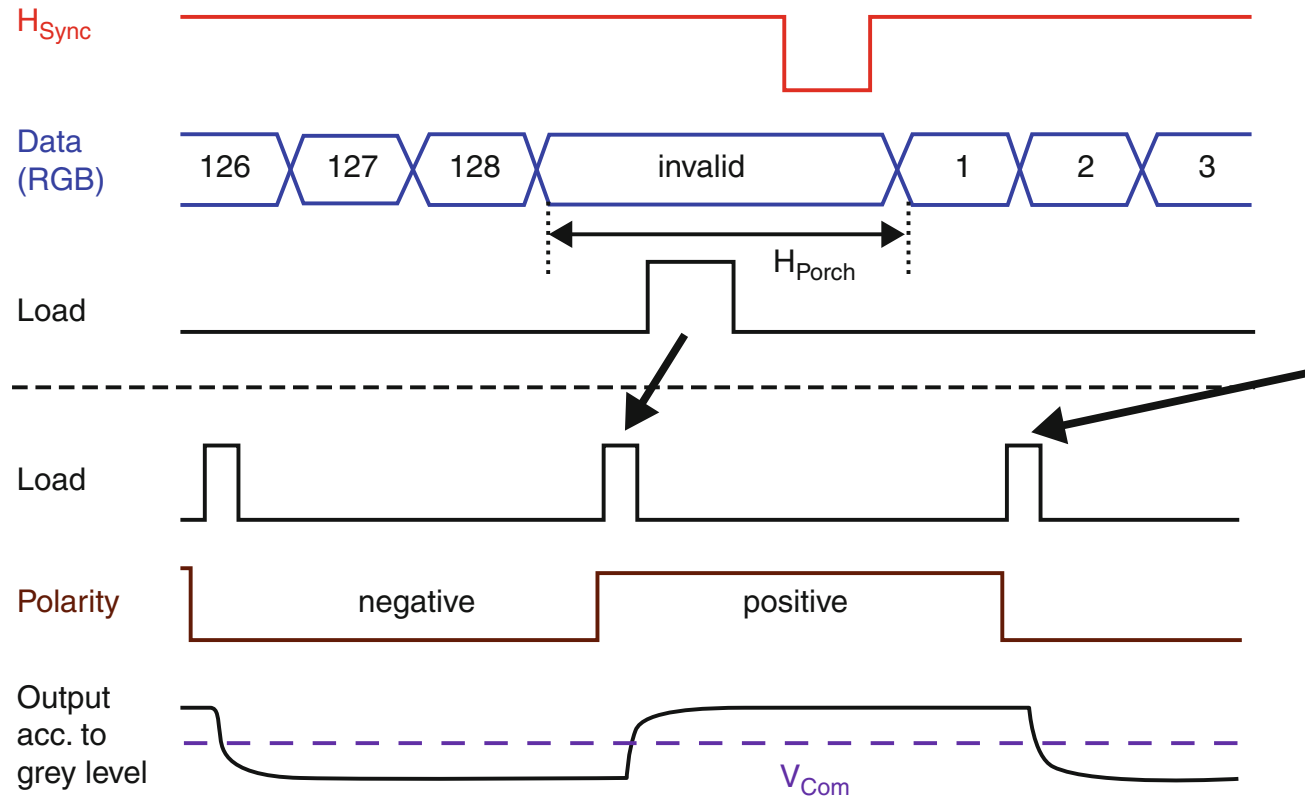


**Fig. 11** Typical timing diagram (clock and some control signals omitted) of an XGA AMLCD column driver

# Power Budget

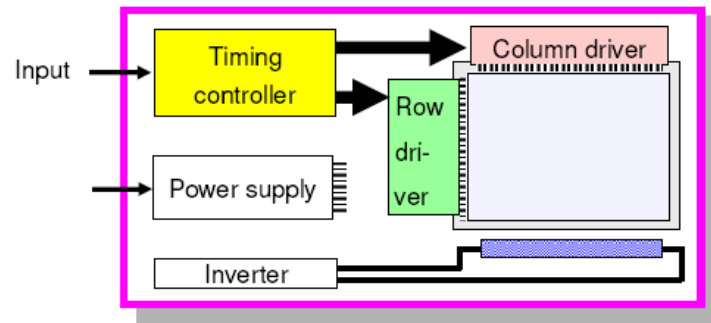

LCD module

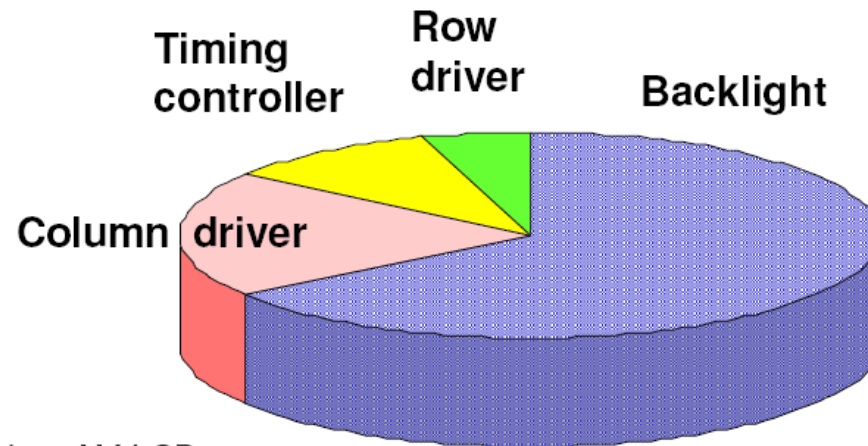Electronics draw ~ 1/3 of total power consumption !



Example for 10.4" VGA Colour AM LCD




## Row/Column Waveforms

### Voltage levels of the LC & Common Electrode



## Row/Column Waveforms


Consider  $N^{\text{th}}$  row

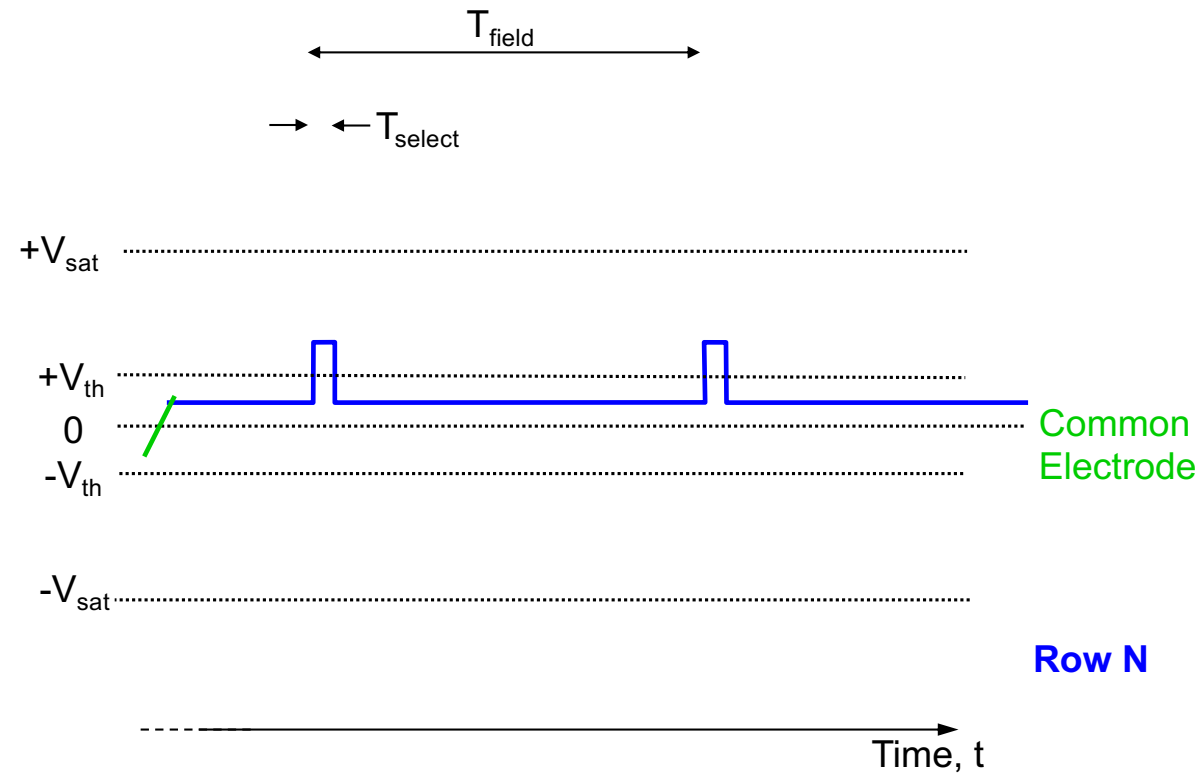
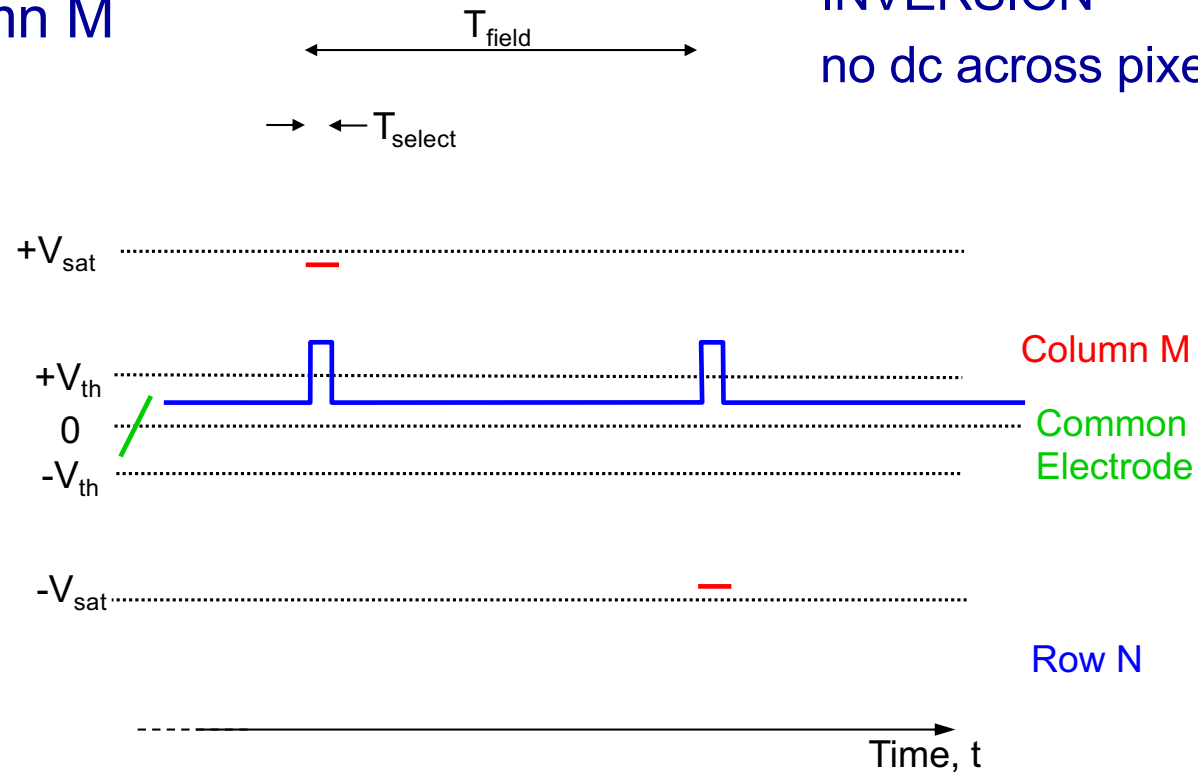
## Row/Column Waveforms


Apply voltage to  
Column M

+ve & -ve voltage  
INVERSION  
no dc across pixel




# Row/Column Waveforms


## Pixel Voltage

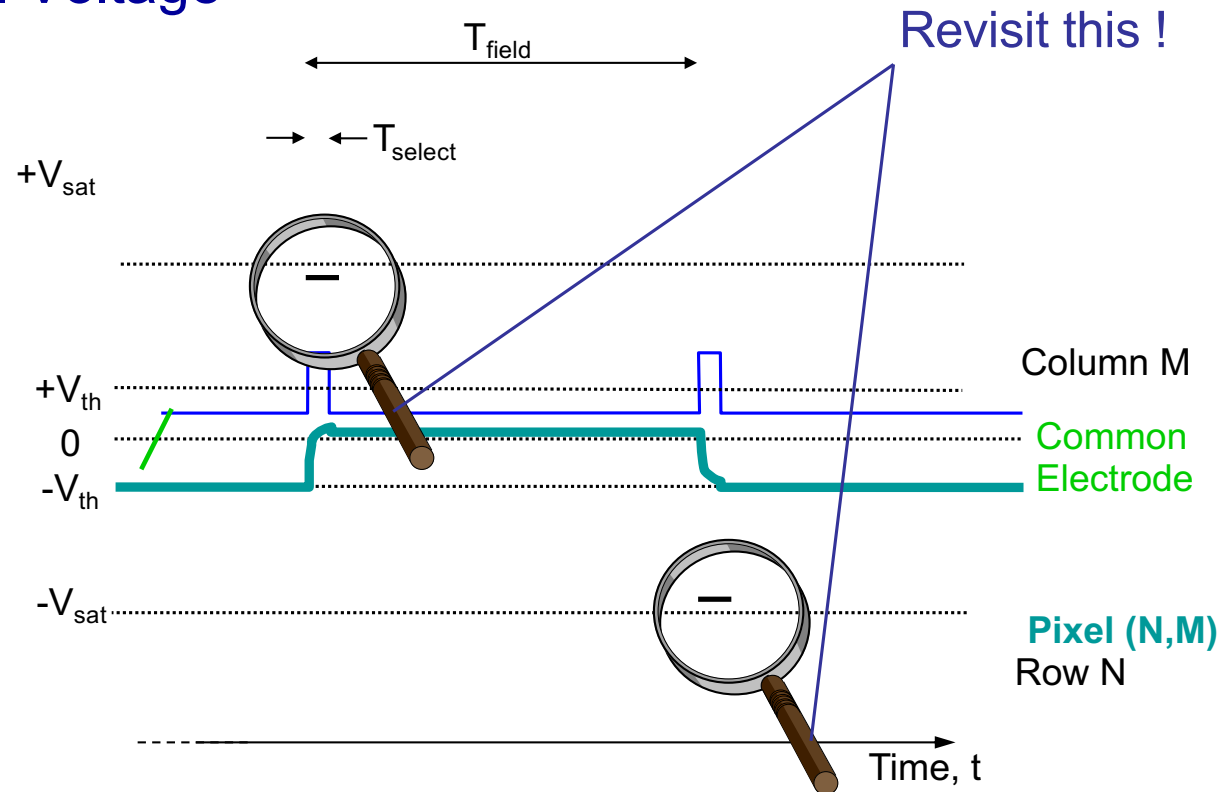


## Row/Column Waveforms

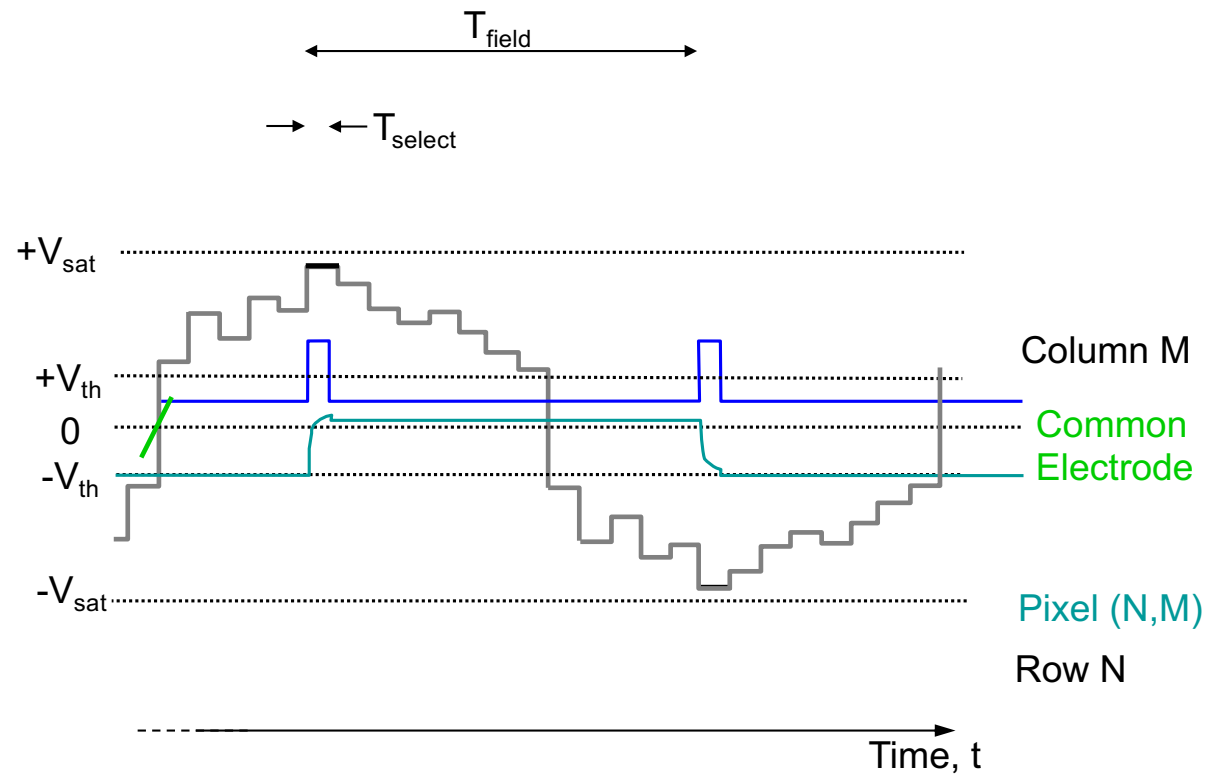


## Row/Column Waveforms

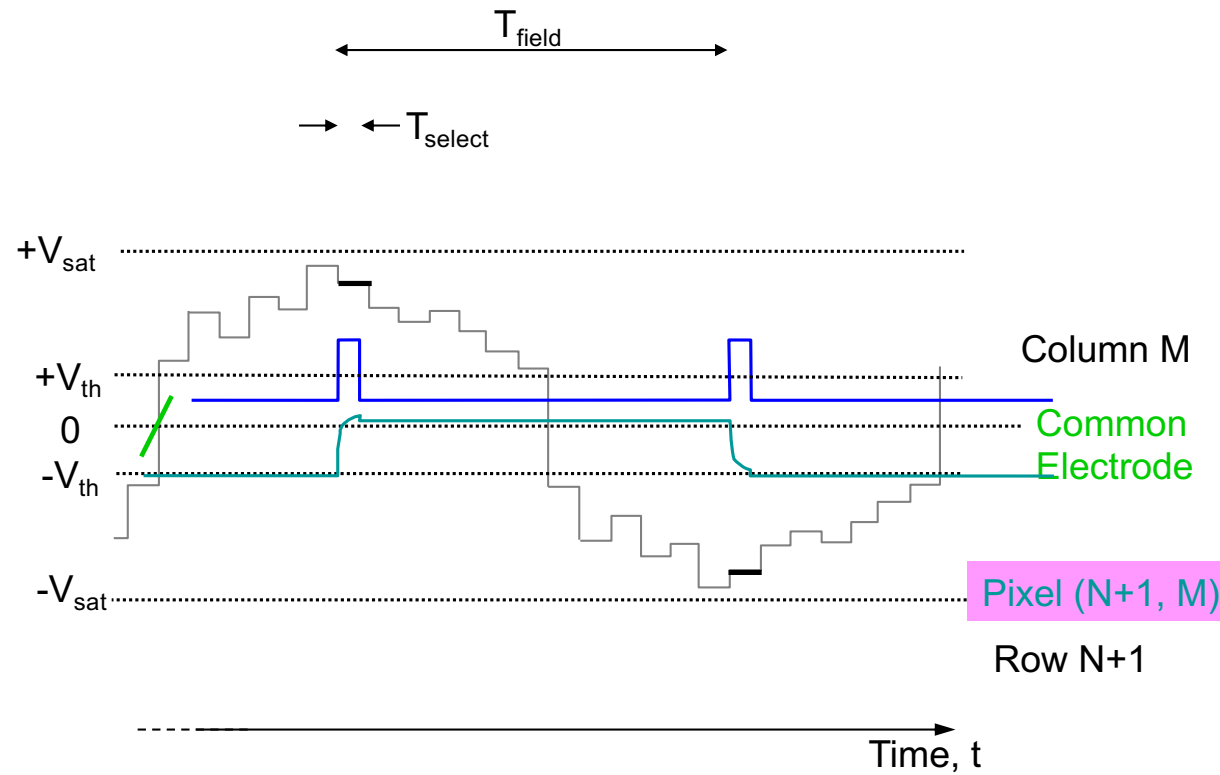

## Row/Column Waveforms

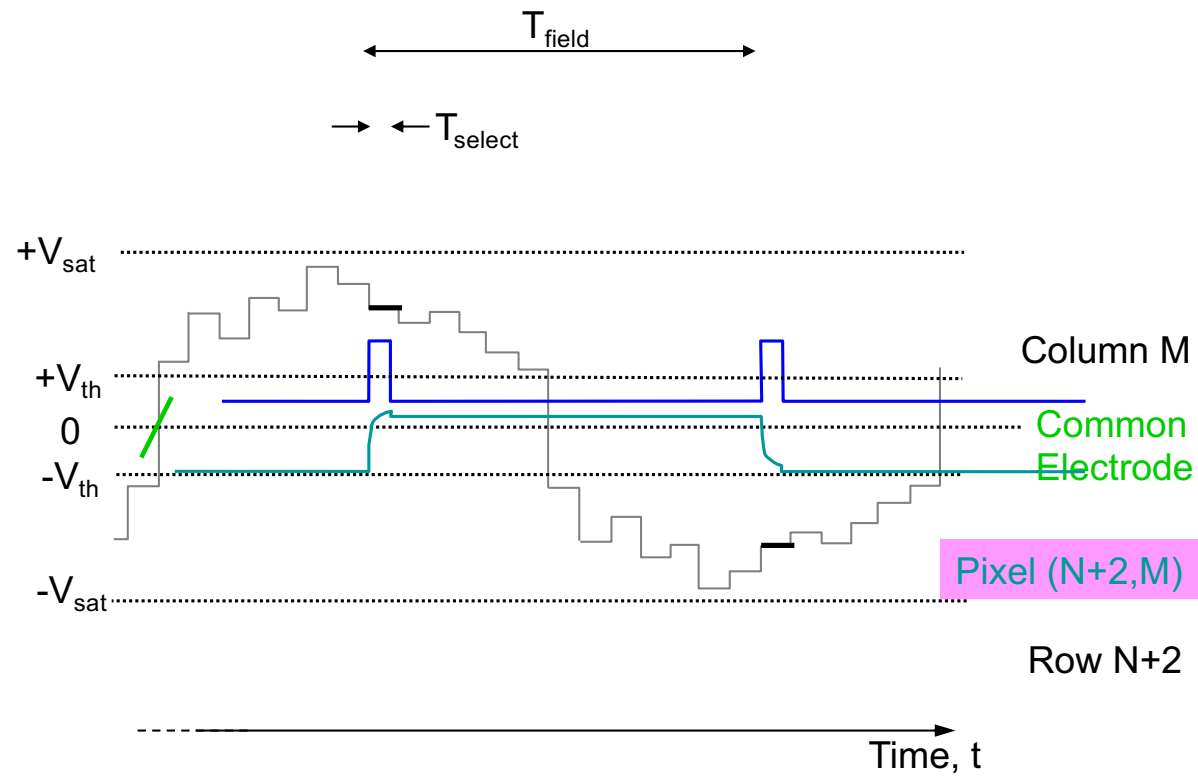

## 1xTFT, 1xC pixel – circuit schematic


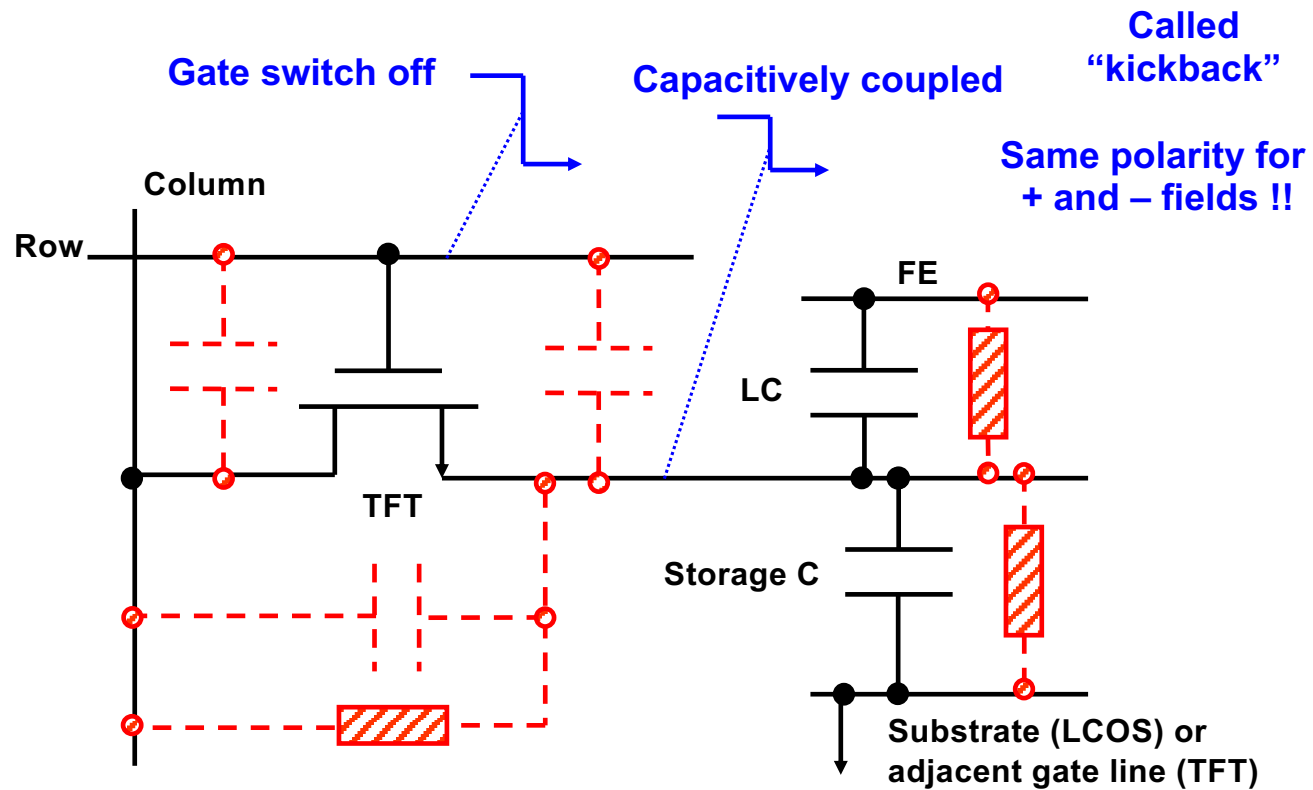


Black / solid is designed-in"

Red / dashed is "parasitic"



## Kickback – the issue

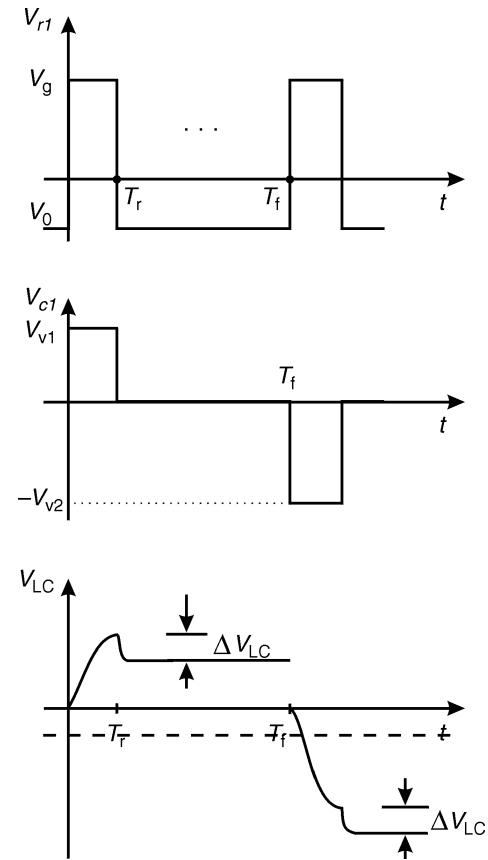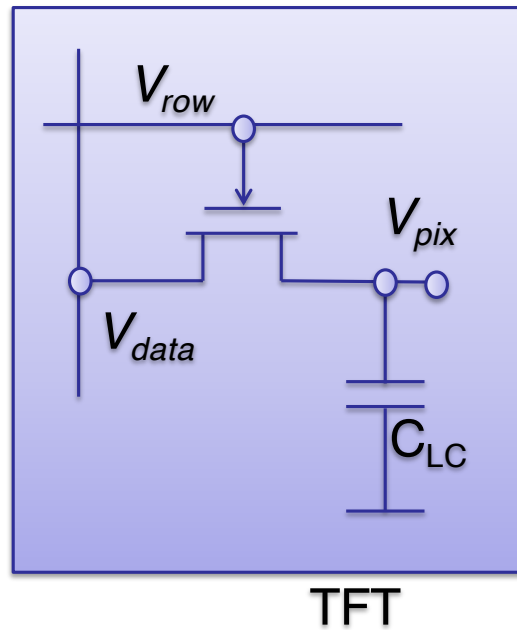

**Figure 14.5** The gate impulses and their effect on the pixel voltage  $V_p$

# Kickback – the problem

## Cause


- Gate drain overlap capacitance
- Gate turn-off edge

## Effects

Asymmetry of + and – field drive voltages

- Net d.c. signal to LC
  - **Electro-chemical degradation**
- Inequality of light level in + and - fields
  - **Visible flicker**

*Exaggerated !*


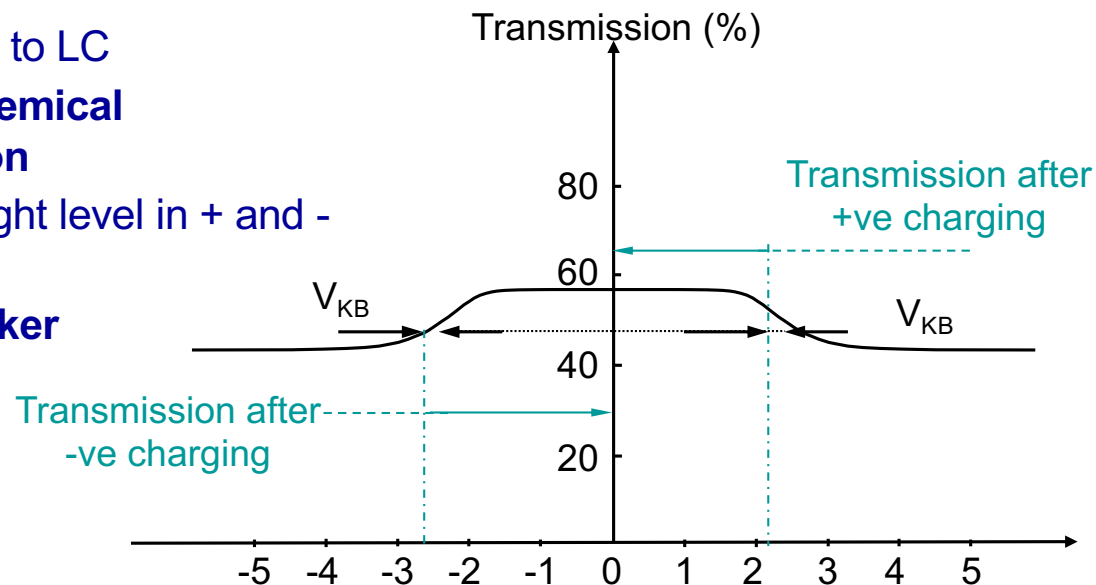


# Kickback - solution
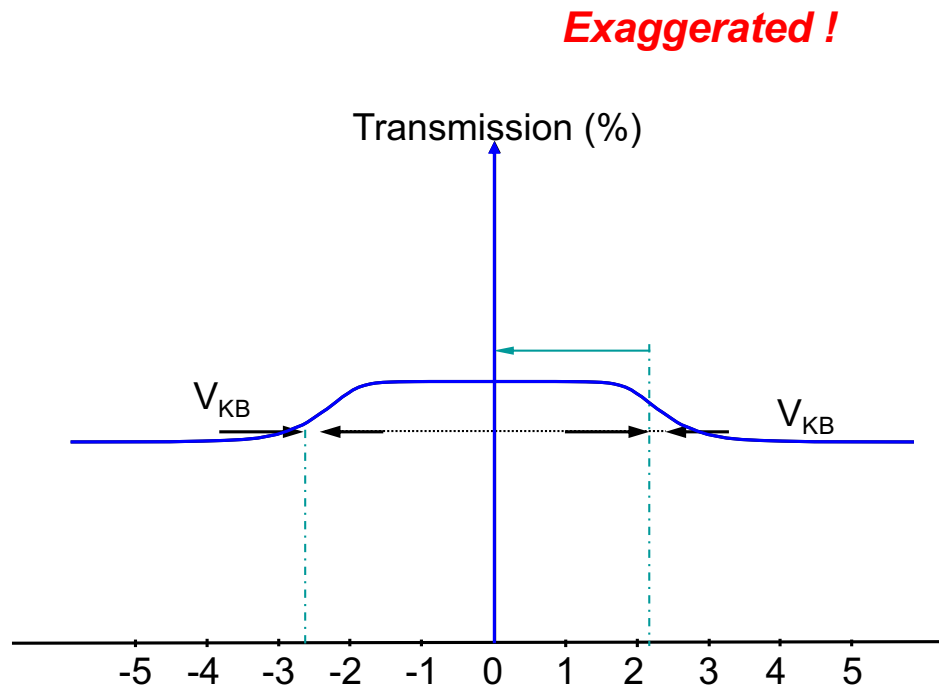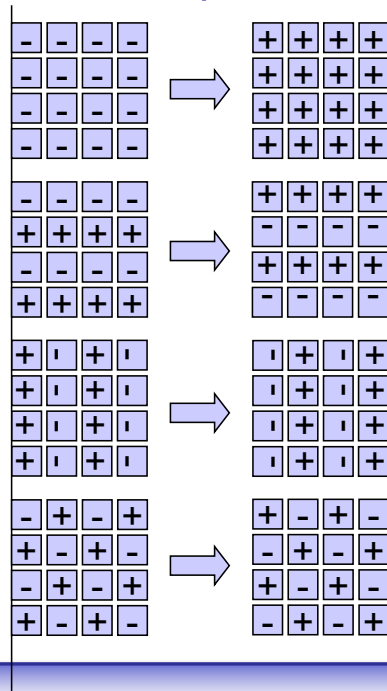
## Improvements

Bias the common electrode to re-balance the symmetry

- DC balance not by field but by row, column or pixel



## External Sources of Information

Handbook of Visual Display Technology **3rd Edition 2020**

<https://link.springer.com/referencework/10.1007/978-3-642-35947-7>

### Part X Fundamentals of Driving

Active Matrix Driving *Blankenbach*

Acknowledgement – some Figures taken from the above source

Not 1<sup>st</sup> edition 2012  
Not 2<sup>nd</sup> edition 2016

### *Mobile Displays: Technology and Applications.*

Ed A. K. Bhowmik, Z. Li, and P. J. Bos © 2008 John Wiley & Sons, Ltd. ISBN: 978-0-470-72374-6

Chapter 9 Advances in Mobile Display Driver Electronics

James E. Schuessler , National Semiconductor, Santa Clara, California, USA